


# solution assginment 10

lahari

January 2021
 
## 1 question

If probability of input data bit(D input) transition in each clock period is 0.3, the average value ( in volts,accurate to two decimal places) of voltage at node X,is 0.8145V.



## 2 answer

In the circuit shown above, a positive edge-triggered D Flip-Flop is used for sampling input

data  $D_{in}$  using clock  $CK$ . The XOR gate outputs 3.3 volts for logic HIGH and 0 volts for logic LOW levels.

The data bit and clock periods are equal and the value of  $\Delta T/T_{CK} = 0.15$ , where the parameters  $\Delta T$  and  $T_{CK}$  are shown in the figure. Assume that the Flip-Flop and the XOR gate are ideal.

If probability of input data bit(D input) transition in each clock period is 0.3, the average value ( in volts,accurate to two decimal places) of voltage at node X,is 0.8145V. volatage at  $X = \frac{T - \Delta T}{T} \cdot (\text{probability}) \cdot (\text{voltage value})$

$$X = 1 - \frac{\Delta T}{T} \cdot (0.3) \cdot (3.3)$$

$$X = (1 - 0.15) \cdot (0.3) \cdot (3.3) = 0.8145V$$