


ASSIGNMENT 11

JAN 5,2021

QUESTION


In the circuit shown below, a positive edge-triggered D Flip-Flop is used for sampling input data D_{in} using clock CK . The XOR gate outputs 3.3 volts for logic HIGH and 0 volts for logic LOW levels. The data bit and clock periods are equal and the value of $\Delta T/TCK = 0.15$, where the parameters ΔT and TCK are shown in the figure. Assume that the Flip-Flop and the XOR gate are ideal.

diagram

 

If probability of input data bit(D input) transition in each clock period is 0.3, the average value (in volts,accurate to two decimal places) of voltage at node X ,is 0.8145V.

diagram

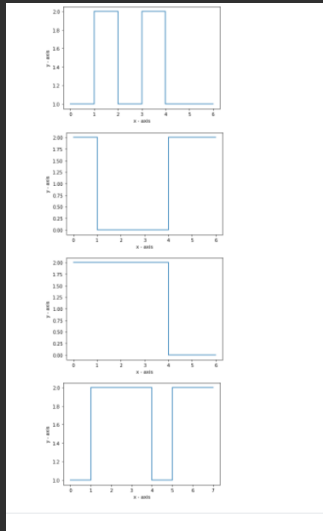

Explanation

voltage at X = $\frac{T - \Delta T}{T} \cdot (\text{probability}) \cdot (\text{voltage value})$

$$X = 1 - \frac{\Delta T}{T} \cdot (0.3) \cdot (3.3)$$

$$X = (1 - 0.15) \cdot (0.3) \cdot (3.3) = 0.8415\text{V}$$